

Rensselaer Polytechnic Institute

VLSI Design

ECSE 4220

Report

Project #1

Inverter Design Assignment

Nikoleta Koleva

TA: Sagnik Nath

Date: 06-Dec-2019

Instructor: Tong Zhang

Table of Contents

Cover Page.....	1
Table of Contents.....	2
Introduction.....	3
Circuit Schematic.....	3
Schematic Simulation Results.....	4
Full Layout.....	6
Design Rule Check (DRC) of the layout.....	6
Layout Extraction and Layout vs. Schematic (LVS) check result.....	7
Post-Layout Simulation.....	9
Simulation Results.....	11
Conclusion.....	11

0. Introduction

Throughout this report, the Cadence IC design tool was used to build and simulate an inverter, using a pfet and an nfet. First, an ideal inverter was built, after which a real-world simulation was compared. The inverter was first tested in ideal circumstances, after which a layout was built upon it but using a real-world setbacks, such as parasitic capacitance and resistance. The responses were then compared and a conclusion was drawn.

1. Circuit Schematic

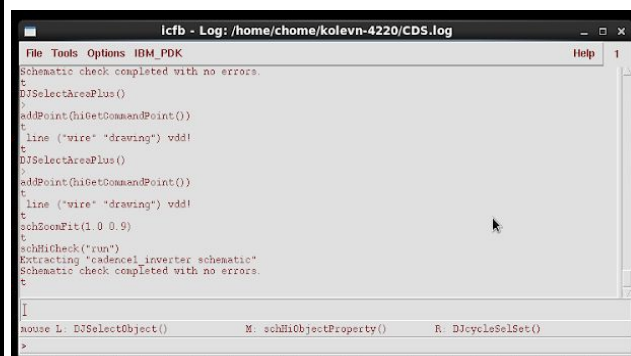
 


Figure 1: Full schematic of inverter circuit Figure 2: Schematic 'Check' results

Figure 1 above displays the inverter circuit initially built in Cadence. To create it, the pfet width was set to 10um and length to 2um. The nfet width was set as 5um and length as 2um. Initially, there were errors given when trying to connect the Input and Output pins but they were fixed, once the source and ground connections were adjusted to be 'vdd!' and 'gnd!' respectively. Figure 2 displays the results obtained by using the 'Check' option to look for any schematic errors. Furthermore, later on LVS was failing due to subc not being added to the schematic. Once this was done, LVS succeeded.

2. Schematic Simulation Results

 


Figure 3: Confirmation of symbol creation

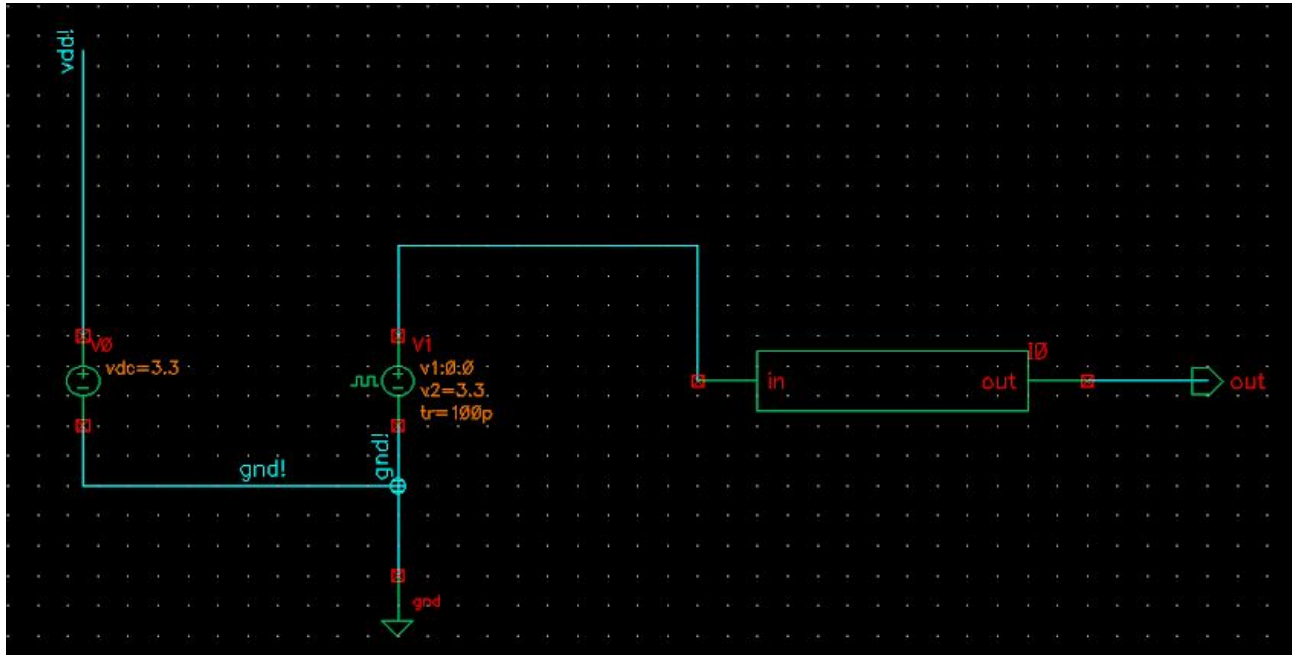


Figure 4: Schematic testbench circuit setup

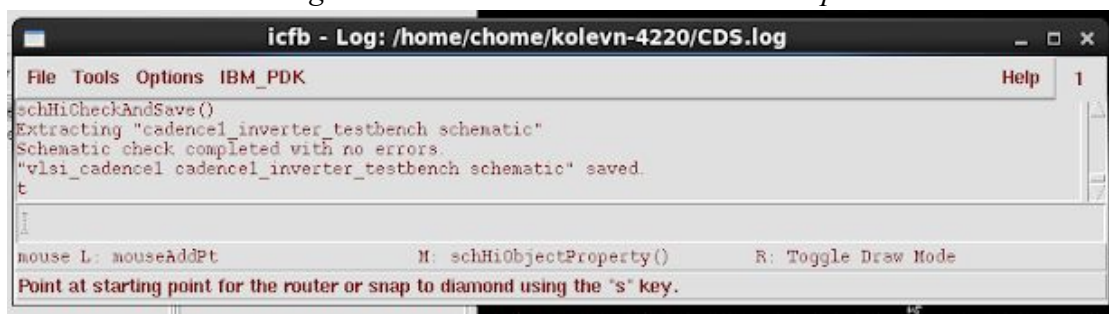


Figure 5: Schematic testbench circuit 'Check and Save' result

For the simulation, a testbench cellview was built to implement the inverter previously built. Additionally, ground, a VDC and a VPULSE sources were added. The VDC DC voltage was set to 3.3V and the VPULSE specs were as follows: DC voltage - 3.3V, Voltage 2 - 3.3V, Rise time - 100ps, Fall time - 100ps, Pulse width - 1ns, Period - 3ns. Once this was built and checked successfully, the simulation was initiated.

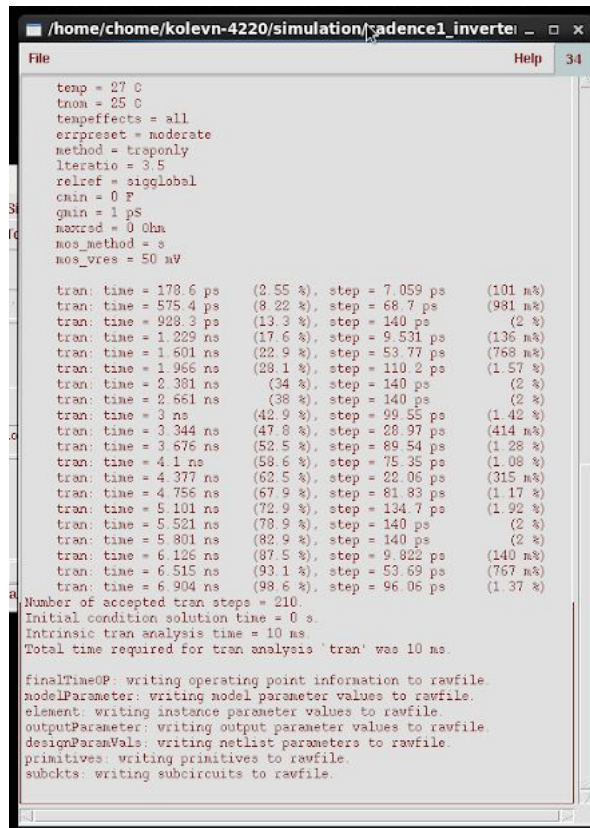


Figure 6: Simulation/Testbench netlist results

 


Figure 7: Schematic simulation result

In Figure 7 above, the result of the simulation can be observed. It was done with a 7ns stop time and done for the schematic file of the inverter. This is the ideal response for the inverter.

3. Full Layout

 


Figure 8: Full layout of inverter circuit

4. Design Rule Check (DRC) of the layout

```
*****
* END OF ERROR REPORT SUMMARY FOR LINE NODE & ORTHOGONALITY *
*****
Start Time = "Dec 9 13:07:57 2019"
Stop Time = "Dec 9 13:07:57 2019"
t
hiSetCurrentForm('ivDRCOptionsForm)
t
hiFormDone(ivDRCOptionsForm)
DRC started at Mon Dec 9 13:08:01 2019
Validating hierarchy instantiation for:
Library: vlsi_cadence1
cell: cadence1_inverter
view: layout
Rules come from library siGe5sm.
Rules path is divaDRC.rul.
Inclusion limit is set to 1000.
Running layout DRC analysis
Plat mode
Full checking.
DRC started ..... Mon Dec 9 13:08:01 2019
completed .... Mon Dec 9 13:08:02 2019
CPU TIME = 00:00:00 TOTAL TIME = 00:00:01
***** Summary of rule violations for cell "cadence1_inverter layout" *****
# errors Violated Rules
1 #INFO: 3 Level Metal (M1-MT+AM) PADS= WIREBOND #
1 #INFO: SiGe-5sm DIVA DRC DECK (05/04/2004) #
2 Total errors found
t
```

Figure 9: DRC check of circuit

In Figure 8 above is the compact cell constructed, which passes DRC, as can be seen in Figure 9 (with only two INFO errors, which are stated as normal/expected in the tutorial document). Initially, there were problems with the contacts, specifically MC_M1 and it wanting to be placed touching the 'OUT' wire when trying to run DRC. When this was done, DRC passed but the compact cell was still incorrect. This was later fixed (as it's a contact for the pc and m1 layers for the 'IN' wire) by aligning it properly on the 'IN' wire. These errors were discovered when running LVS check later, as they did not show up in DRC.

5. Layout Extraction and Layout vs. Schematic (LVS) check result

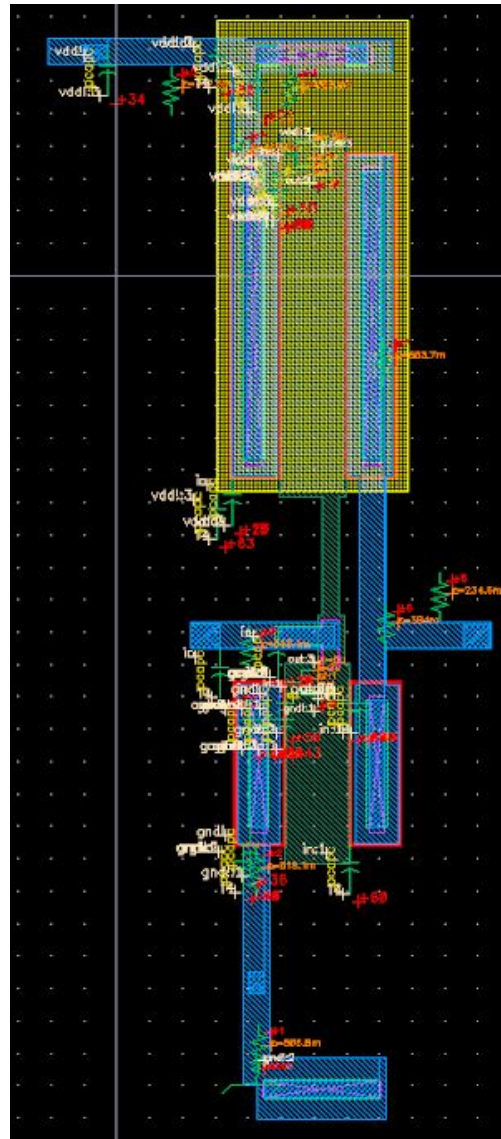


Figure 10: Extracted view of the layout

```
For layer sub.dev :
  1 shapes encountered.
  1 subck aulvs sig55m devices well formed.
48 pcapc aulvs sig55m parasitics created
1 pcapnw aulvs sig55m parasitics created
0 pcapnw aulvs sig55m parasitics created
0 pcapnw aulvs sig55m parasitics created
Extraction started ..... Mon Dec 9 13:16:50 2019
completed ..... Mon Dec 9 13:16:51 2019
CPU TIME = 00:00:00 TOTAL TIME = 00:00:01
***** Summary of rule violations for cell "cadence1_inverter layout" *****
Total errors found: 0
saving rep vlsi_cadence1/cadence1_inverter/extracted
t
```

Figure 11: Extraction error results

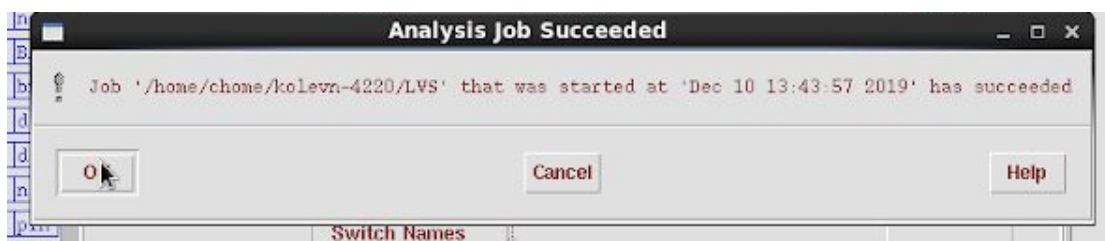


Figure 12: LVS check results

The layout extraction can be seen in Figure 10 above. It came out with no errors. Afterwards, the LVS check was run on the layout and succeeded once the layout and schematic problems were resolved. Those included added a missing subc to the schematic and fixing the contact issues for the 'IN' output. Once these were fixed, the layout passed through DRC and was re-extracted, the LVS check was successful, as can be observed in Figure 12.

```

@(#)SCDS: LVS.exe version 5.1.0 06/20/2007 02:10 (cicln03) $
Command line: /cad/cds/ic5.141USR5/tools.lnx86/dftII/bin/32bit/LVS.exe -dir /home/chome/kolevn-4220/LVS -l -t /home/chome/kole
Like matching is enabled.
Using terminal names as correspondence points.

Net-list summary for /home/chome/kolevn-4220/LVS/layout/netlist
count
5      nets
4      terminals
1      nfet
1      subc
1      pfet

Net-list summary for /home/chome/kolevn-4220/LVS/schematic/netlist
count
5      nets
5      terminals
1      nfet
1      subc
1      pfet

Terminal correspondence points
N1      N2      gnd!
N3      N5      in
N2      N7      out
N0      N0      vdd!

Devices in the netlist but not in the rules:
pcapacitor pdiode presistor
Devices in the rules but not in the netlist:
subcx res singlewire coupledwires npn1a npn2a npn1b1a npn1b2a glpnpa
nfetm pfetm pfetm varm pinm pin_ringm ebdm nimm niam dcapm rnsres
nsresm pbdresm pbsresm frdtresm frnsresm riresm niam pfetm pbsresx
frnsresx pbsres riresx duo1 duo2 gnpv vdiu pind tl2 tl4 resShort
frnsres mosvar rires pbsres npn1 npn2 npn1b1 npn1b2 pin pin_ring ebd
var ind indline glpnp esd bondPad npn npn1b dcap frdtres niam nsres
pbdres rnsres

The net-lists match.

                                layout schematic
                                instances
un-matched                      0          0
revised                          0          0

```

Figure 13: Netlists match check

Lastly, before attempting the post-layout simulation, the si.out file was checked to ensure that the netlists of the schematic and layout matched. This was initially not the case due to the wrong contacts on the 'IN' wire. Once fixed, the netlists matched as desired, as seen in Figure 13.

6. Post-Layout Simulation

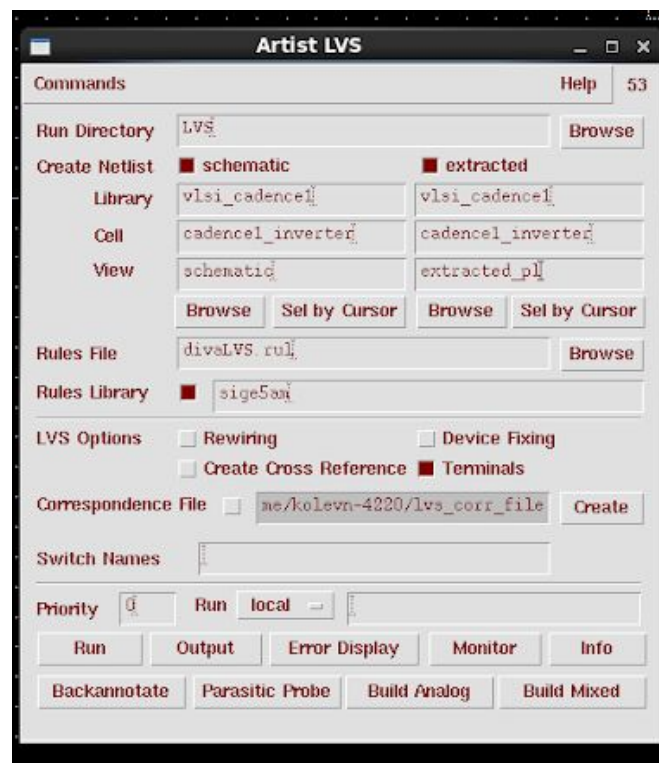


Figure 14: After redoing extraction, rerunning LVS and using 'Build Analog' for analog_extracted

(cont. on next page)



Figure 15: analog_extracted view

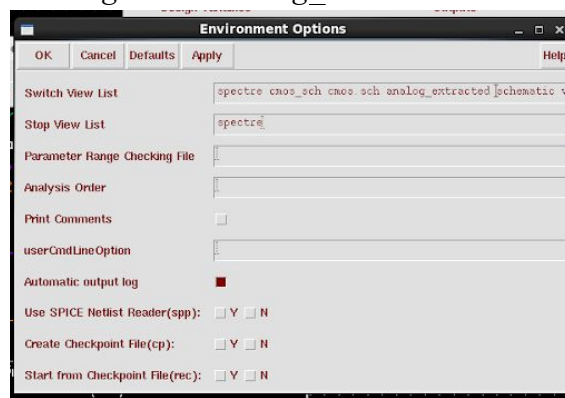


Figure 16: Changing view list in testbench simulation environment by adding analog_extracted for it to refer to that file

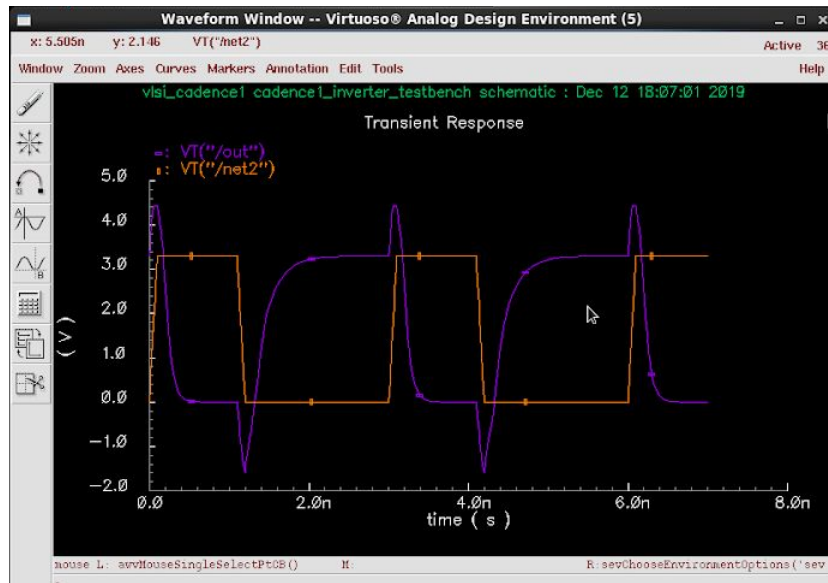


Figure 17: Post-layout simulation result

When preparing for the post-layout simulation, the extracted file had to be updated first to ensure that it was using the latest version of the layout. Once this was done, LVS was rerun (successfully) after which the ‘Build Analog’ option was selected, which can be seen in Figure 14. After this was done, the testbench circuit was opened once more and in the environment options, ‘analog_extracted’ was added prior to schematic for the simulation to access the extracted view, rather than the schematic file, as can be observed in Figure 16. Finally, a simulation was run, which can be seen in Figure 17.

7. Simulation Results

The results of the post-layout simulation look pretty similar when first observed but it can also be seen that the analog simulation has shorter rise and fall time compared to the original ideal simulation. These faster changes between states occur due to the parasitic capacitance and resistance added in the extracted layouts. They are problems that do not have to be taken into account when simulating an ideal inverter but should be considered for real-world simulations, as they can impact a bigger circuit’s response. To see the changes more easily, the input frequency can be increased in order to see a more obviously different output response.

8. Conclusion

Through this exercise, it can be concluded that while parasitic capacitance and resistance change the ideal response, they do not fundamentally change how the pre-analog circuit behaves. Though the rise and fall time are altered, the output response keeps its form, meaning the circuit does not fundamentally change its function. This response is due to parasitic elements is expected, based on the parasitic element definition studied in class. However, these slight changes should be taken into account when building real-world circuits, as they can change a circuit’s response, leading to unexpected or unwanted results.